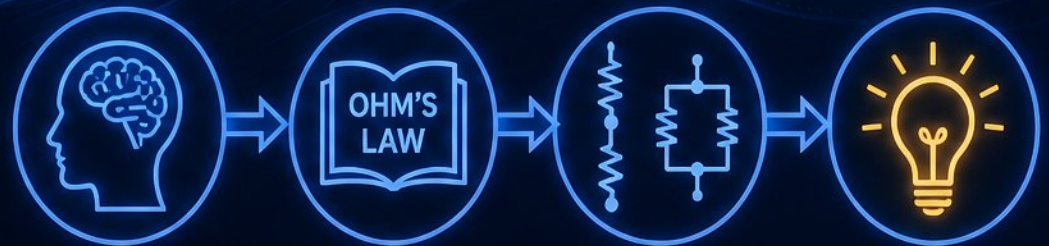


Introduction to Electric Circuits: Current, Voltage, and Resistance

- Build accurate conceptual models for circuits, not just memorize formulas
- Current, voltage, and resistance are the foundation of all circuit analysis
- Journey from mental models through Ohm's Law to series/parallel patterns
- Directly confronting common misconceptions: 'constant current' and 'current consumption'
- Adopting a scientific model means letting go of intuitive but incorrect ideas



Confronting the Misconceptions We Bring

- ✓ Battery is not a source of constant current
- ✓ Charge is never 'used up' by components
- ✓ Voltage and current are distinct concepts
- ✓ Adopt the cyclic simultaneous model for circuits
- ✓ Let go of ideas that don't hold up to evidence



The Non-Negotiable: What a Circuit Absolutely Needs



- A closed, continuous conducting loop is required for charge to flow



- Switches open/close the loop; conductors vs. insulators matter



- Circuit as a completely filled, continuous chain or hose loop




- Battery is an energy pump, not a source of fresh charge




Electric Current: It's Not Consumed, It's a Cycle

- Current (I) = charge flow rate past a point, measured in amperes (A); $1\text{ A} = 1\text{ C/s}$
- Conventional current flows (+) to (−); free electrons drift the opposite way
- Electron drift speed ($\sim 1\text{ m/hour}$) vs. near-light-speed signal propagation
- Charge carriers are never "used up"; current is identical everywhere in a single loop

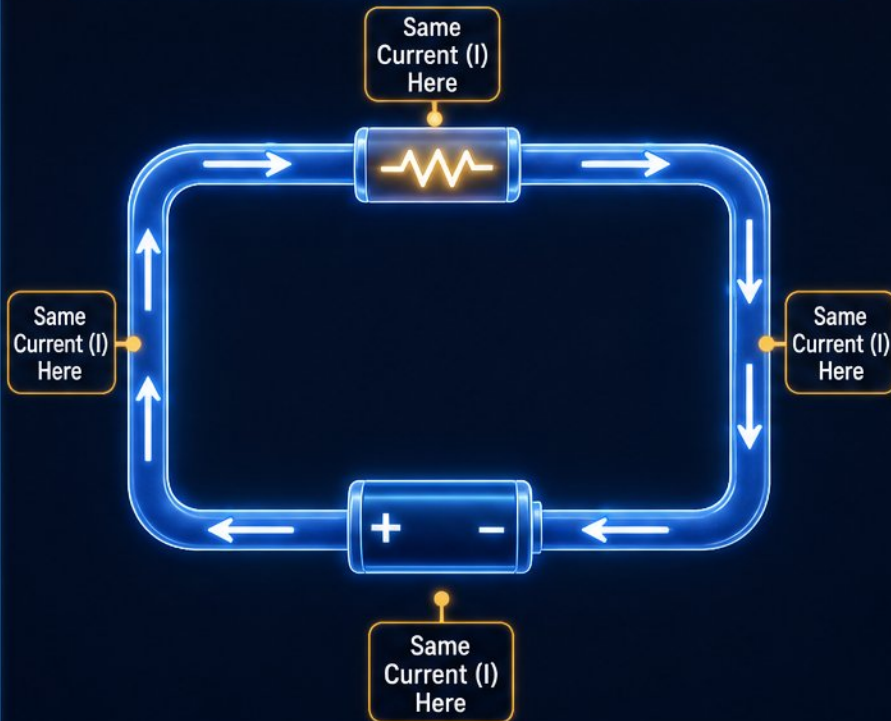CURRENT IS IDENTICAL EVERYWHERE IN A SINGLE LOOP



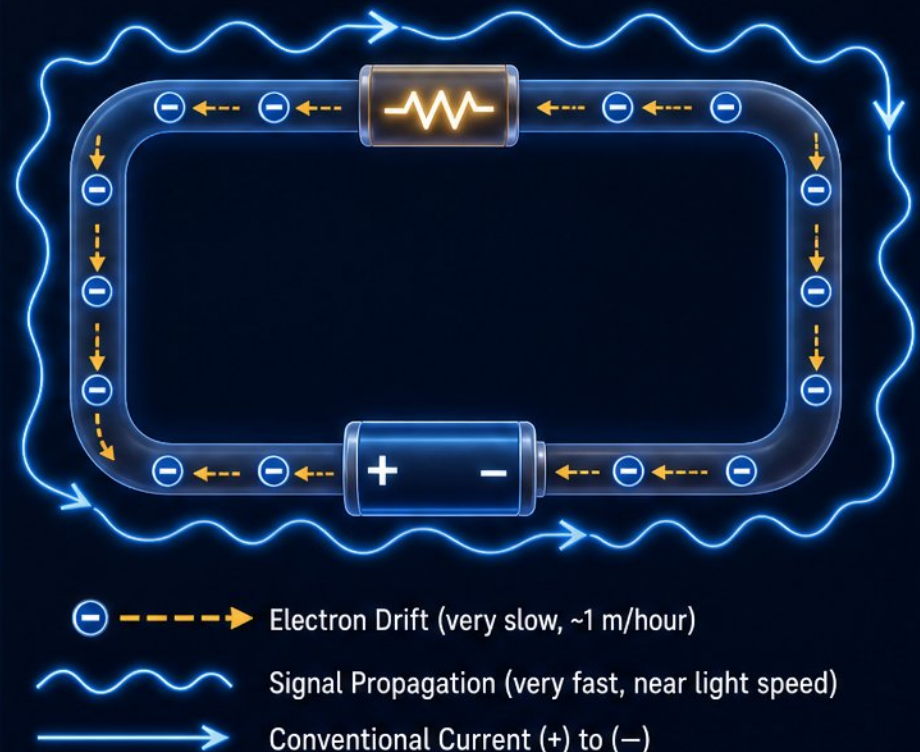
ELECTRON DRIFT (SLOW) vs. SIGNAL PROPAGATION (FAST)



Voltage:

The Reason for the Push


- **Voltage (V)** is an electric pressure difference that causes charge to flow, measured in volts across two points.
- The battery acts as an '**energy pump**' creating a pressure difference in a completely filled pipe system.
- **EMF** is the pump's ideal pressure; **terminal voltage** is the actual pressure available under load.
- Everyday levels: 1.5V (AA cell), 9V (rectangular battery), 120/230V mains. **Voltmeters connect in parallel.**

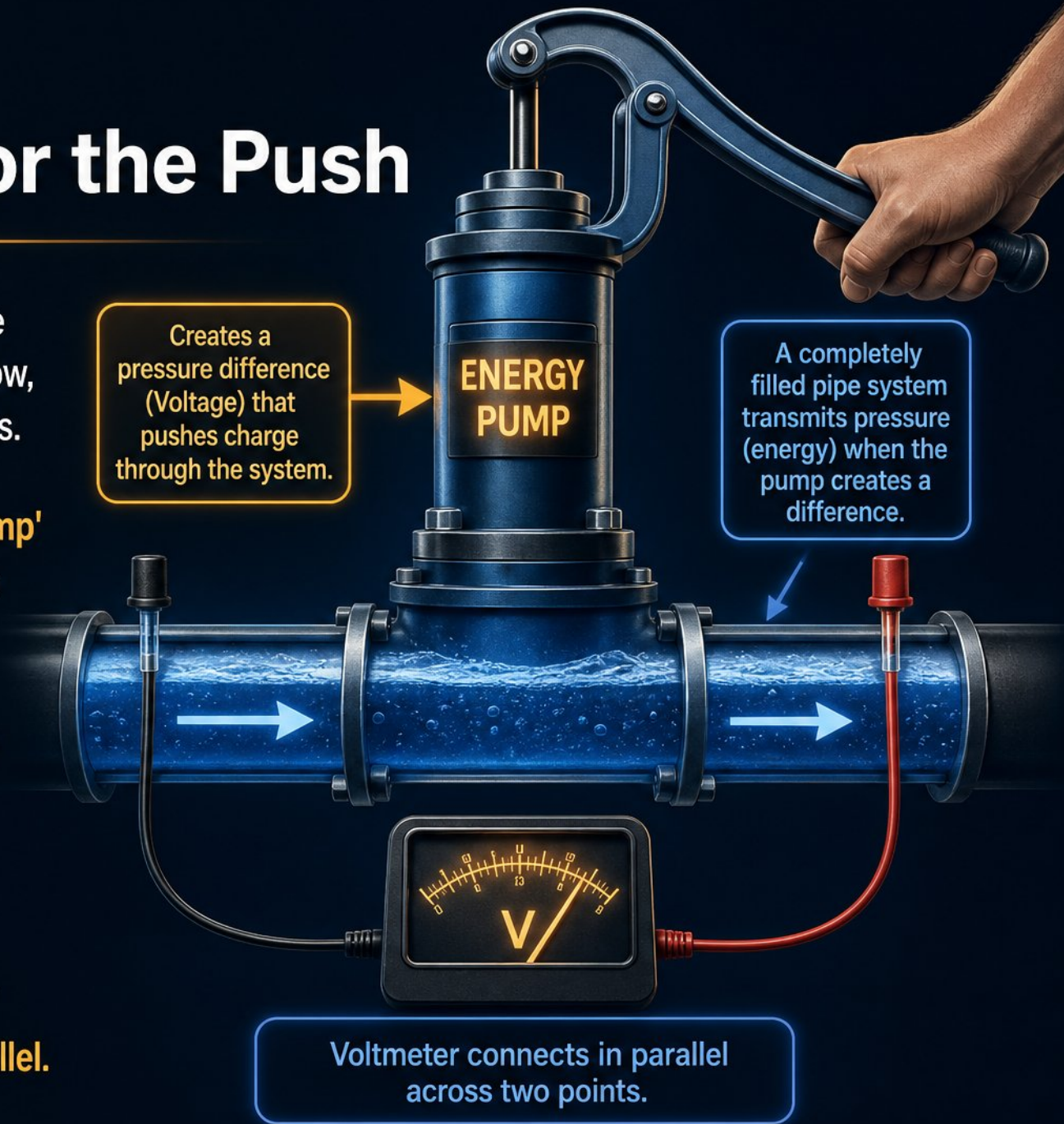


Resistance: The Opposition to Flow

- - Resistance (R) limits current; arises from collisions in the conductor's atoms
- - Longer = more R ; thinner = more R ; depends on material resistivity
- - Water analogy: thick pipe vs. tight constriction = resistor
- - Everyday scale: wire $\sim$ few Ω , insulation $\sim$ $M\Omega$

WATER ANALOGY

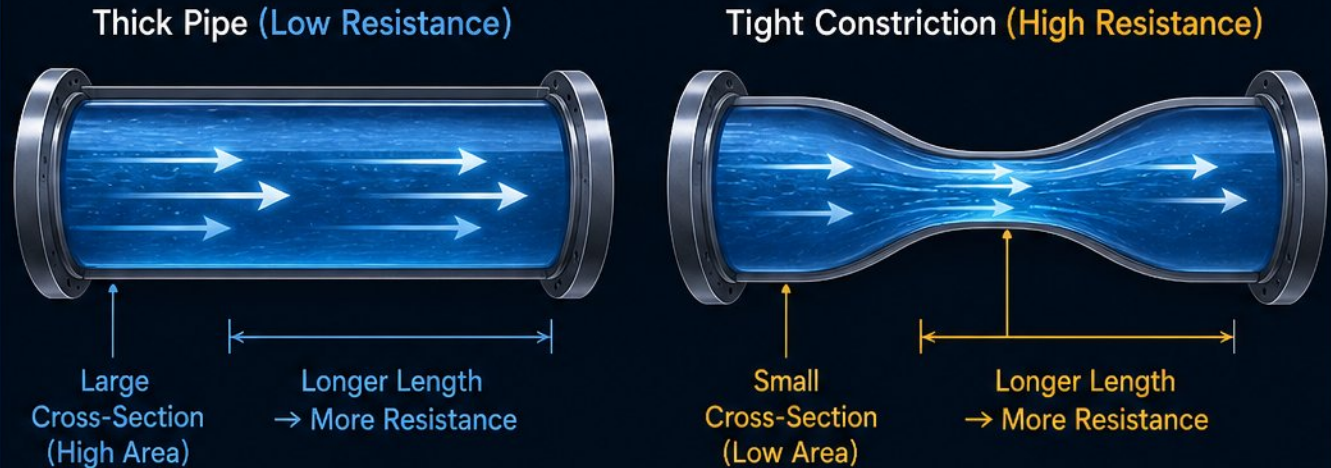

COLLISIONS IN THE CONDUCTOR'S ATOMS


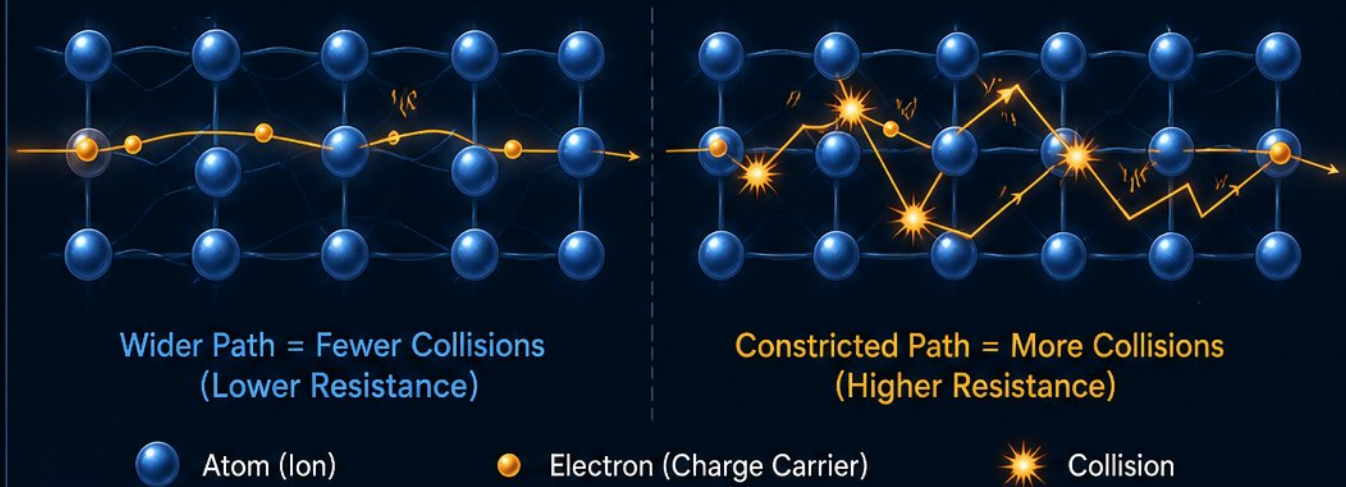


Ohm's Law:

The Unifying Relationship


- The quantitative link: $V = I \times R$
(Current = Voltage / Resistance).
- Current is directly proportional to voltage; double V , I doubles.
- Current is inversely proportional to resistance; halve R , I doubles.
- I - V graphs for ohmic resistors form a straight line; slope is $1/R$.
- Worked example: A 120V supply powers a 192Ω lamp
→ $I = 0.625$ A.

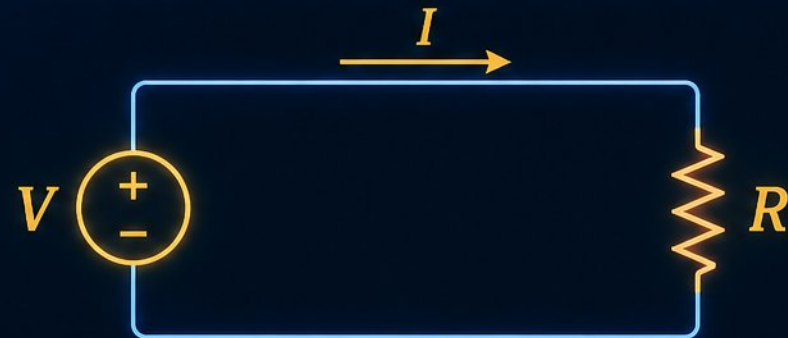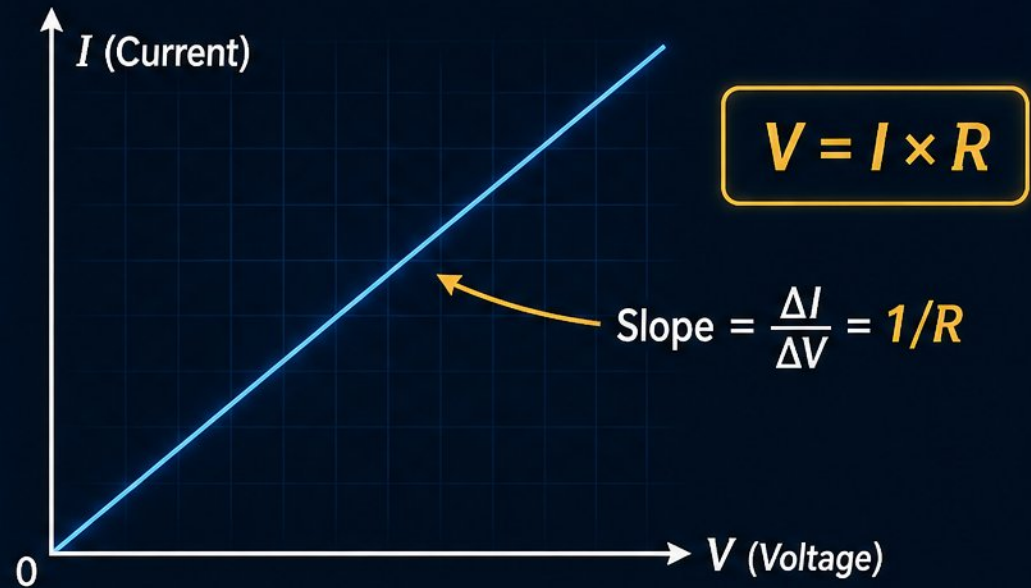I - V CHARACTERISTIC OF AN OHMIC RESISTOR



Getting Hands-On: Your Ohm's Law Laboratory

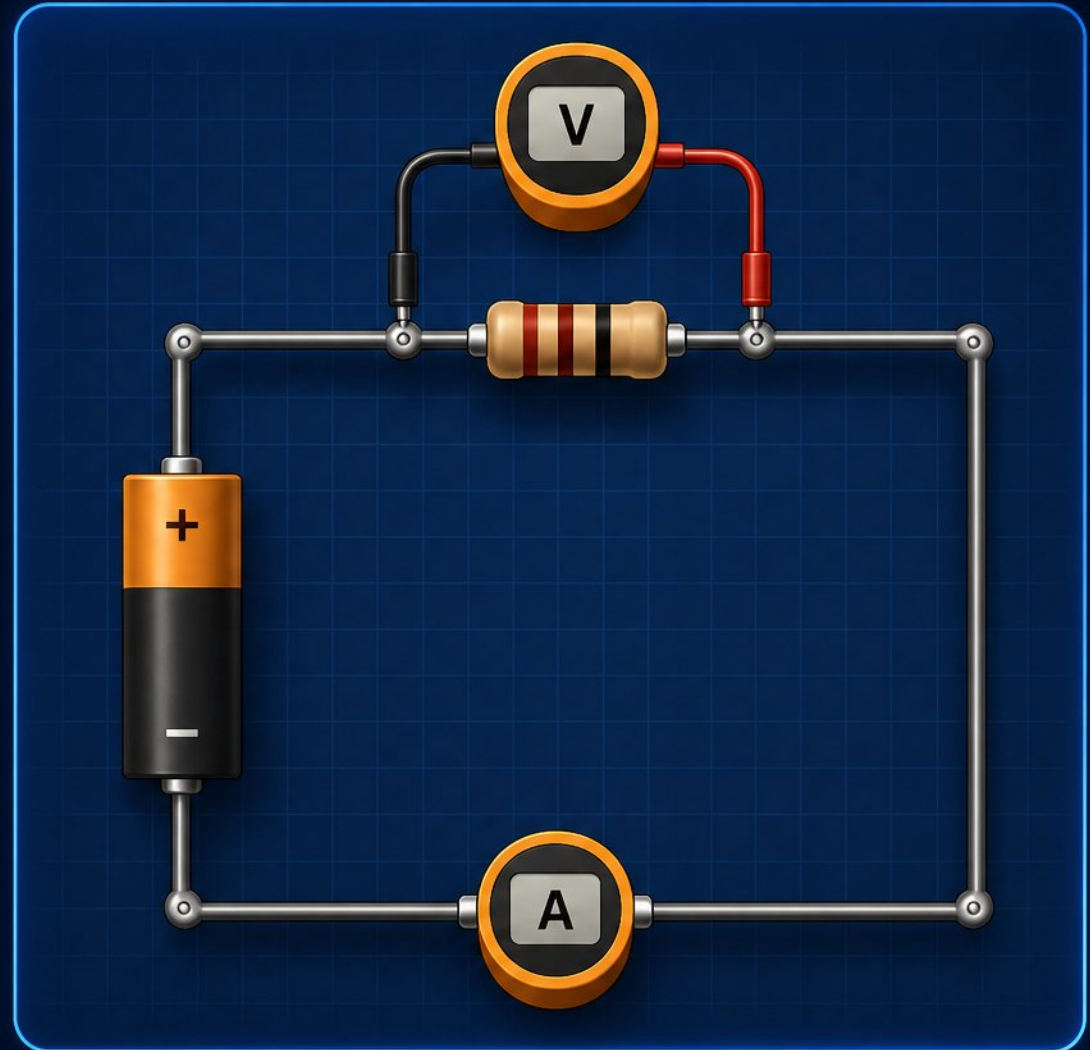- - Build a simple DC circuit with a battery, resistor, and wires
- - Measure voltage with a voltmeter placed in parallel
- - Measure current with an ammeter connected in series
- - Plot collected V-I data to find the line's slope
- - Confirm the slope matches the resistor's known ohmic value



Series Circuits: A Single Path for Current



- Only **one path** for current: current is identical through every component.



- **Voltage divides**: the supply voltage is split among series components.




- **Higher resistance** gets a larger share of the voltage budget.



- Adding more bulbs increases total resistance, **lowering total current**.



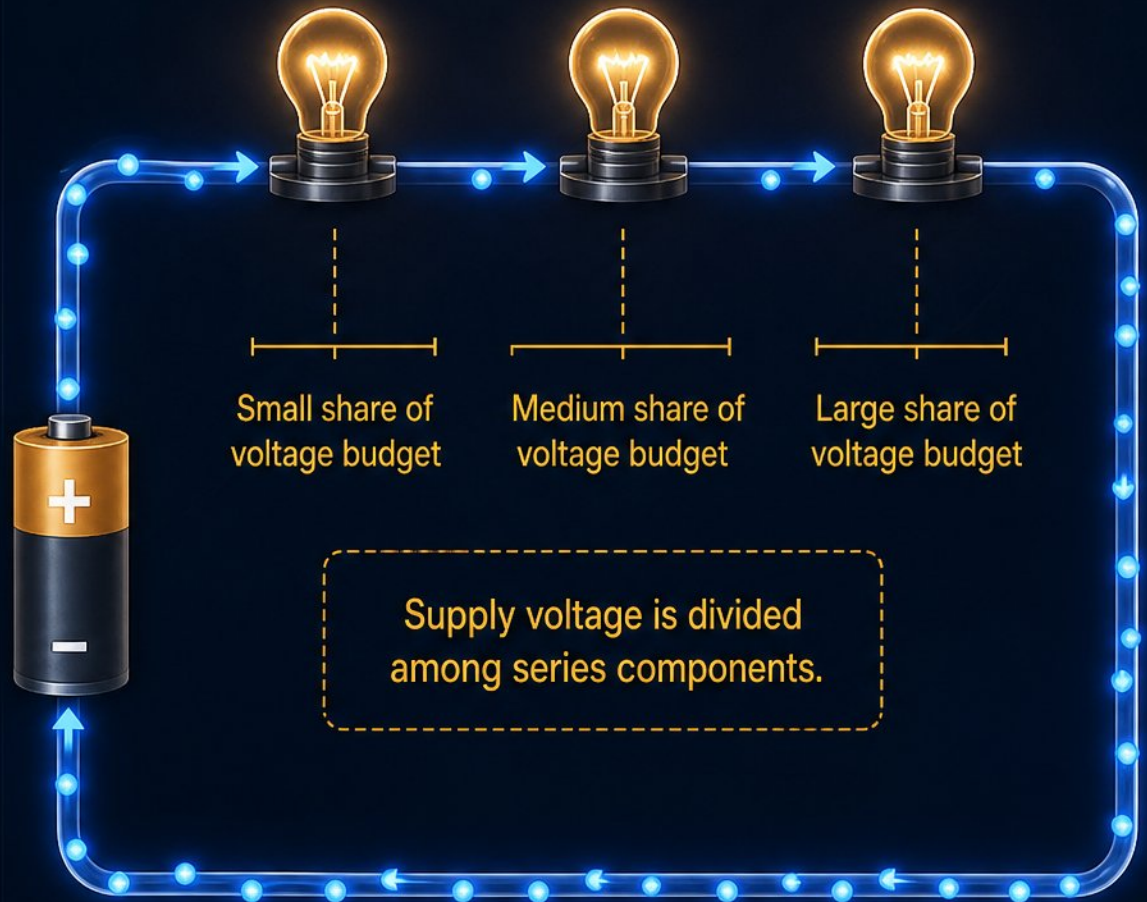- An open circuit anywhere **breaks the entire path** — all or nothing.




Blue dots and arrows represent the flow of charge (current).

Parallel Circuits:

Multiple Independent Paths

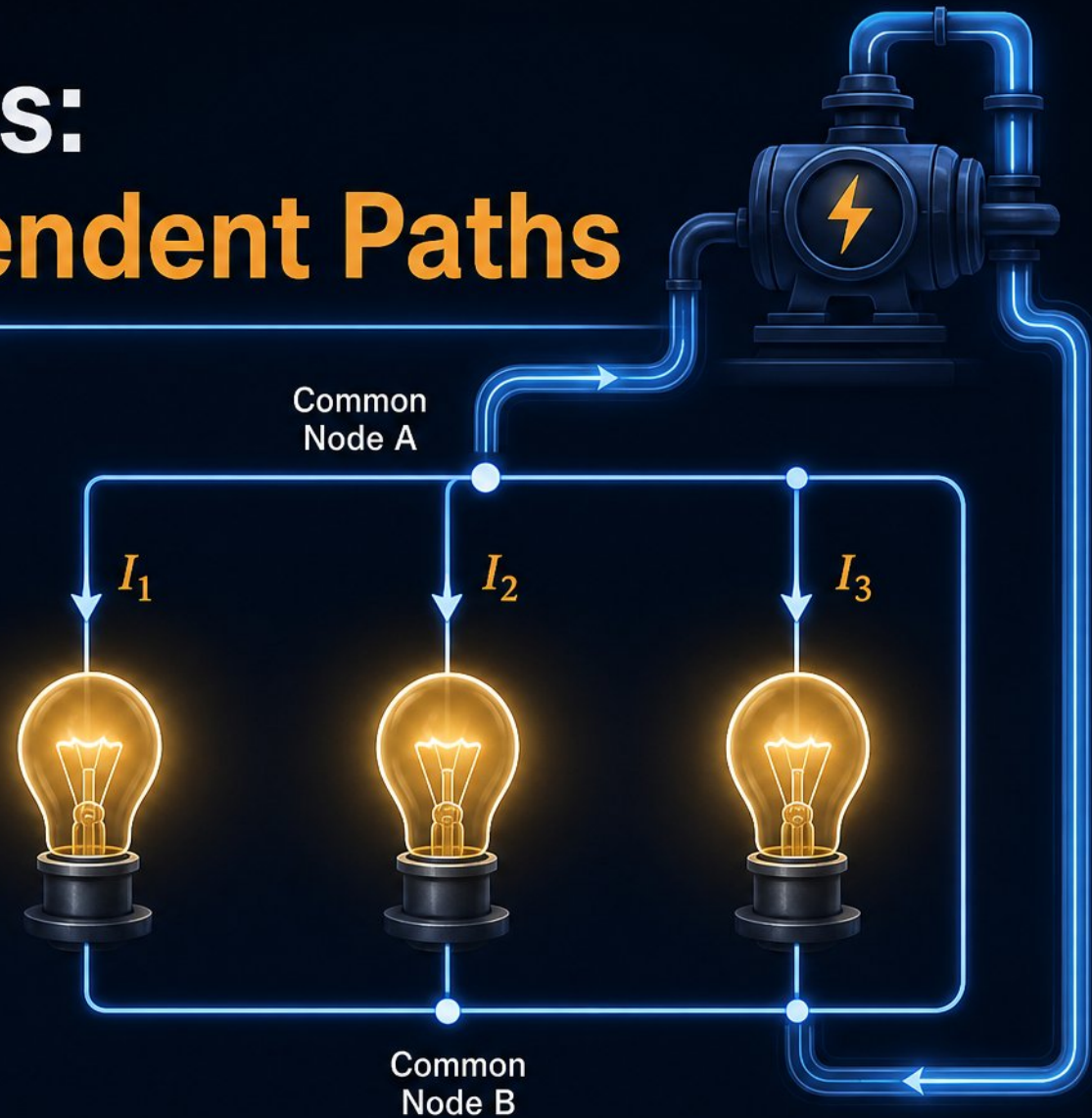- Parallel branches share two common nodes, creating multiple paths for current.
- Voltage is identical across every parallel branch.
- Total current equals the sum of branch currents (Kirchhoff's Current Law).
- Adding a parallel path reduces total resistance and increases total draw.
- Identical bulbs in parallel shine equally bright, but drain the battery faster.





Total current equals the sum of branch currents.

$$I_T = I_1 + I_2 + I_3$$

Diagnosing Brightness: Applying the Model to Lamps

- Brightness reflects power ($P=V \times I$), not current or voltage alone. High-wattage bulbs have lower filament resistance.
- Series puzzle: the lower-wattage bulb (higher R) dissipates more power and glows brighter.
- Parallel puzzle: the higher-wattage bulb (lower R) draws more current, dissipates more power, and glows brighter.
- Use the PhET sim to test predictions—never rely on brightness heuristics without full circuit analysis.

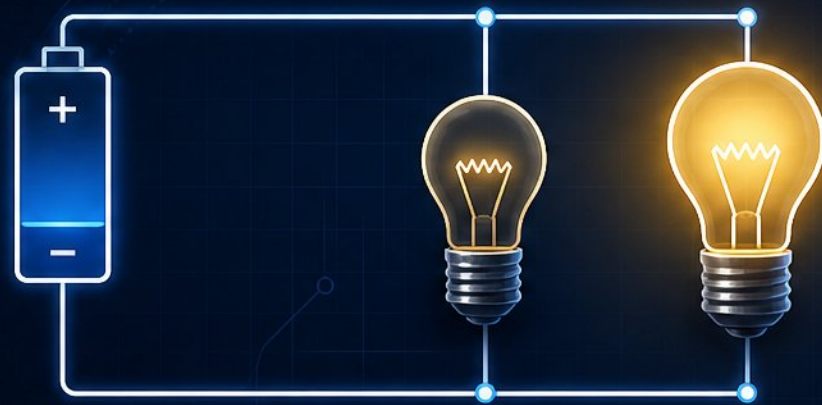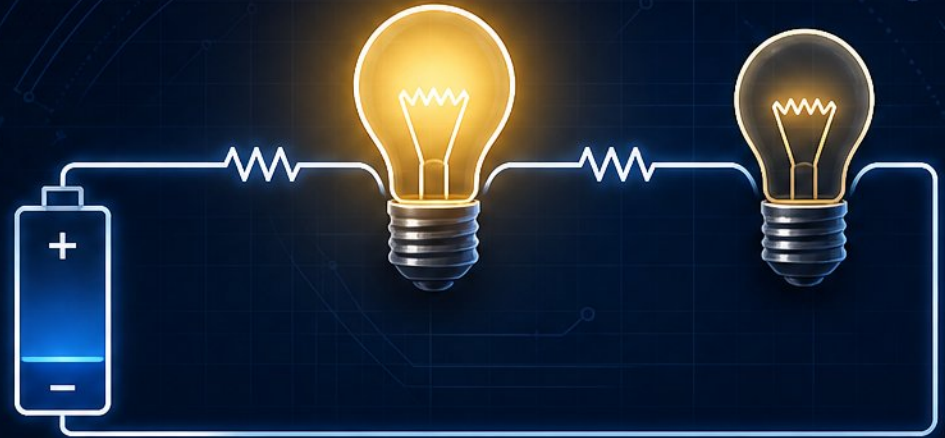

Energy and Power:

Where the Circuit Does Work

- Power (**P**) is the rate of energy transfer; $P = V \times I$
- Joule heating: resistors convert electrical energy into thermal energy
- Appliance labels tell a story: **V**, **A**, and **W** are connected
- Example: A **120V, 1800W** hair dryer draws **15A**
- Overloading parallel circuits draws too much total current—dangerous



Troubleshooting and Testing Your Mental Model



- Before calculating, **predict**: will the change increase or decrease V , I , or P ?



- **Don't confuse** "voltage across" with "current through"; know open vs. short.



- **Use a voltmeter** to diagnose a dead circuit; a wire has negligible voltage drop.



- **Self-check**: Adding a third parallel bulb increases total current, dims none.



- **Rely on Ohm's Law** and conservation of charge, not intuition.



Summary, Key Takeaways, and Your Next Steps



- A closed path is mandatory; current is conserved, never consumed.



- Voltage drives the flow; resistance limits the flow.




- Ohm's Law ($V=IR$) bridges qualitative models and quantitative analysis.



- Series and parallel patterns are the building blocks of all circuits.



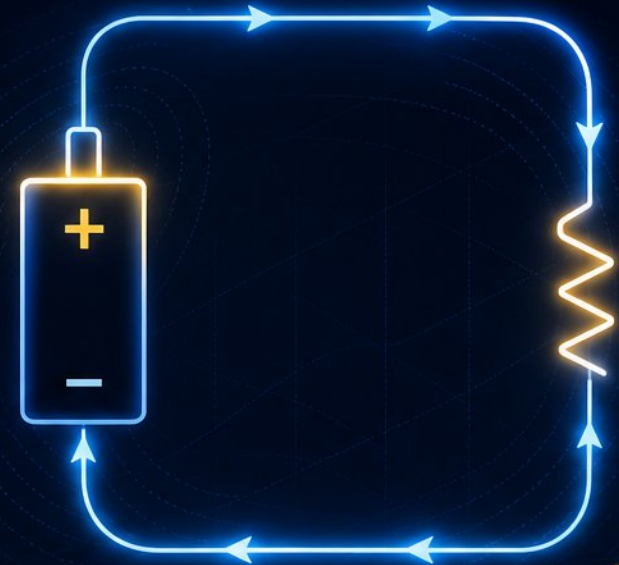- These core concepts extend to capacitors, semiconductors, and AC systems.



PersonWise.

PersonWise • AI digital-human course platform



Scan the code or click anywhere to watch this course live, with voice Q&A

personwise.ai/t/23b0f214/public